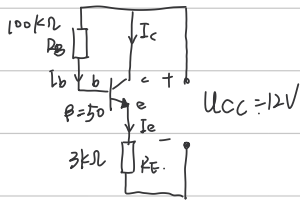


3.2.2


(1) 静态工作点:



$$\begin{cases} U_{CC} = I_B R_B + U_{BE} + I_E R_E \\ I_C = \beta I_B \\ I_B + I_C = I_E \\ U_{CC} = U_{CE} + I_E R_E \end{cases}$$

$$\Rightarrow \begin{cases} I_B = 44.66 \mu A \\ I_C = 2.23 mA \\ U_{CE} = 5.17 V \end{cases}$$

(2)

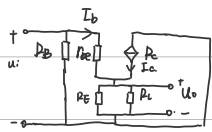

$$r_{be} = 200 + (1 + \beta) \frac{26}{I_E} = 783 \Omega$$


$$A_u = \frac{I_E (R_E \parallel R_L)}{I_B r_{be} + I_E (R_E \parallel R_L)} = 0.987$$

$$r_i = \frac{u_i}{I_B} = \frac{u_i}{I_B + \frac{u_i}{R_B}} = \frac{I_B r_{be} + I_E (R_E \parallel R_L)}{I_B + \frac{I_E (R_E \parallel R_L)}{R_B}} = 38.3 k\Omega$$

$$r_o = R_E \parallel \frac{r_{be}}{1 + \beta} = 15.3 \Omega$$

3.3.1

(1)

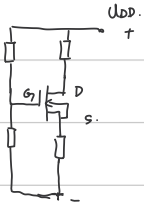

$$U_G = U_{DD} \frac{R_2}{R_1 + R_2} \quad U_S = R_S I_D$$


$$I_D = I_{DSS} \left(1 - \frac{U_{GS}}{U_{GS(off)}} \right)^2$$

$$U_{GS} = U_G - U_S = -0.0943 V$$

$$I_D = 0.4245 mA$$

$$U_{DS} = U_{DD} - I_D (R_D + R_S) = 5.57 V$$

(2)

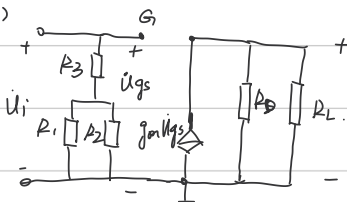


$$A_u = -g_m \frac{R_D R_L}{R_D + R_L} = -6.35$$

(3)

$$r_i = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 2.075 M\Omega$$

$$r_o = R_D = 22 k\Omega$$

3.4.3

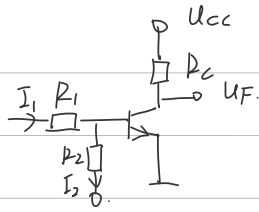

$$I_{cs} = \frac{U_{cc} - U_{ces}}{R_c} = 12 \text{ mA}$$

$$I_{BS} = I_{cs} / \beta = 0.12 \text{ mA}$$

$$I_B \geq I_{BS}$$

$$I_B = I_1 - I_2 = \frac{U_B - U_{BE}}{R_1} - \frac{U_{BE} - (-U_{EB})}{R_2} \geq I_{BS}$$

$$\therefore U \geq 8.45 \text{ V}$$

4.1.1

$$(1) (A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}B + \bar{A}C + CB + CC) = (A+B)(\bar{A}B + \bar{A}C + C) = (A+B)(\bar{A}B + C)$$

$$= A\bar{A}B + AC + B\bar{A}B + BC = \bar{A}B + AC + BC = \bar{A}B + AC + BC + A\bar{A}$$

$$= (\bar{A}+C)(A+B)$$

(2)

$$\bar{A}B + BD + D(A+\bar{A}) + CDE = \bar{A}B + D + CDE = \bar{A}B + D$$

(3)

$$= AB(C+\bar{C}) + \bar{A}\bar{B} + \bar{A}B\bar{C} = AB\bar{C} + AB\bar{C} + \bar{A}\bar{B} + \bar{A}B\bar{C} = B\bar{C}(A+\bar{A}) + \bar{A}\bar{B} + AB\bar{C}$$

$$= AB\bar{C} + \bar{A}\bar{B} + B\bar{C}$$

(4)

$$\overline{AB + BC + CA} = \overline{ABC + \bar{A}\bar{B}\bar{C}}$$

$$\overline{AB + BC + CA} = \overline{AB} \cdot \overline{BC} \cdot \overline{CA} = (\bar{A} + \bar{B})(\bar{B} + \bar{C})(\bar{C} + \bar{A}) = (\bar{A}\bar{B} + \bar{A}\bar{C} + \bar{B}\bar{C})(\bar{C} + \bar{A})$$

$$= \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} \quad (\bar{A}\bar{A} = 0)$$