

2.2.2 已知图 2.08 电路的参数及电流如图中所示,若 U_s 增加 2 V,则 I 为多少?


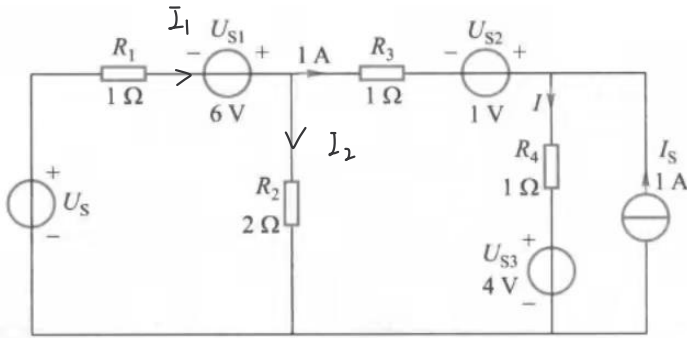


图 2.08 习题 2.2.2 电路


使用叠加原理,考虑 $U_s = 2V$.

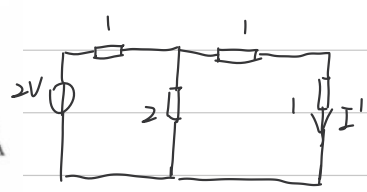


$$I' = \frac{2}{1 + \frac{2}{2}} \times \frac{1}{2} A = 0.5 A$$

$$\therefore I = 1 A + 1 A + 0.5 A = 2.5 A$$

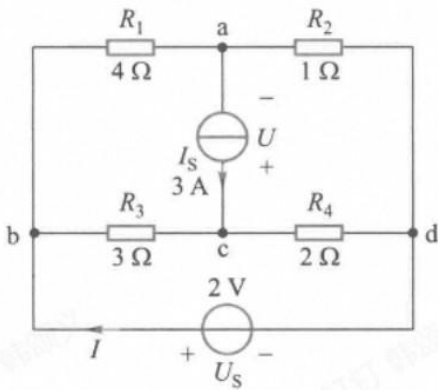2.2.3 试用叠加定理求图 2.05 所示电路中流过 U_s 的电流 I ,图中元件参数和题 2.1.5 相同。




当只有 U_s 时.

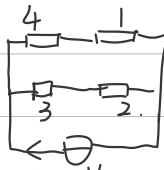

$$I' = \frac{2V}{5/2\Omega} = 0.8 A$$

当只有 I_s 时.

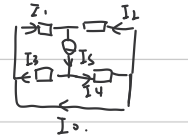

$$I_3 + I_4 = I_s$$

$$I_3 R_3 = I_4 R_4$$

$$I_1 R_1 = I_2 R_2$$

$$I_1 + I_2 = I_s$$


$$\therefore I_0 = 0.6 A - 1.2 A$$

$$= -0.6 A$$


$$\therefore I = I_0 + I' = 0.2 A$$

2.2.7 在图 2.05 所示电路中,将 U_s 以外的电路看成一个二端网络。试用等效电源定理求流过 U_s 的电流 I 。

等效电源

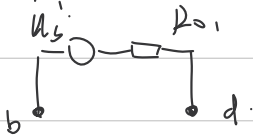


R_0 :

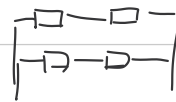


$$R_0 = \left(\frac{1}{5} + \frac{1}{5} \right)^{-1} = 2.5 \Omega$$

$U_{s'}$:

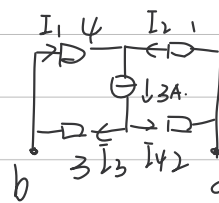

$\Rightarrow$

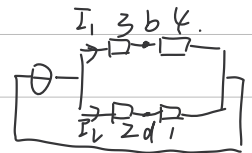

$$7I_1 = 3I_2$$

$$I_1 = 0.9 A$$

$$I_1 + I_2 = 3 A$$

$$I_2 = 2.1 A$$

$$\therefore U = 4 \times 0.9 V - 2.1 V = 1.5 V$$

$$\therefore I = \frac{U_s - U_{s'}}{R_0} = \frac{2 - 1.5}{2.5} A = 0.2 A$$

2.2.8 如图 2.12 所示以 a、b 为端点的二端网络中, 含有电流控制电流源 $20I_2$ 。试求: (1) 当 $R_3 = 10 \text{ k}\Omega$ 时的开路电压 U_{oc} 和等效电阻 R_0 ; (2) 当 $R_3 = \infty$ 时的开路电压 U_{oc} 和等效电阻 R_0 。


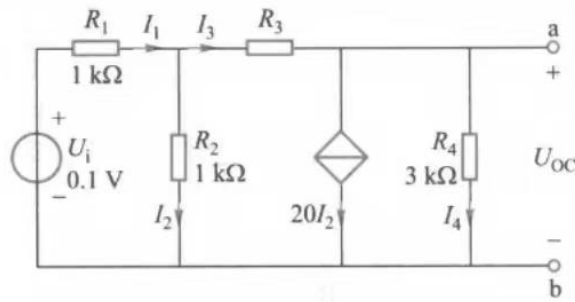


图 2.12 习题 2.2.8 电路

(1)

$$\begin{cases} I_3 = 20I_2 + I_4 \\ I_1 = I_2 + I_3 \\ U_i - I_1 R_1 - I_3 R_3 - I_4 R_4 = 0 \\ U_i - I_1 R_1 - I_2 R_2 = 0 \end{cases} \quad \begin{cases} I_1 = 0.086 \text{ mA} \\ I_2 = 0.01494 \text{ mA} \\ I_3 = 0.07011 \text{ mA} \\ I_4 = -0.2287 \text{ mA} \end{cases} \quad \therefore U_{oc} = I_4 R_4 = -0.0861 \text{ V}$$

将 U_i 置零, 可简化电路:

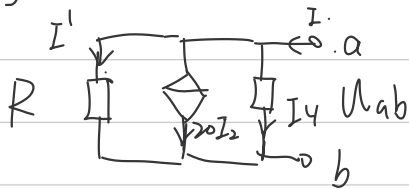

由分流关系得: $I' = 2I_2$

$$\begin{cases} I = I_4 + 20I_2 + 2I_2 \\ I'R = I_4 R_4 \end{cases} \quad \begin{aligned} R_4 &= \frac{U}{I_4} \\ R_0 &= \frac{U}{I} = \frac{2}{29} \Omega \\ &\approx 0.06897 \Omega \end{aligned}$$

$$R = R_3 + \frac{R_1 R_2}{R_1 + R_2} = 10.5 \text{ k}\Omega$$

(2)

当 $R_3 = \infty$, 即视为开路。

$$I_2 = \frac{U_i}{R_1 + R_2} = 0.05 \text{ mA} \quad \begin{aligned} U_{oc} &= I_4 R_4 = R_4 \times (-20I_2) \\ &= -3 \text{ V} \end{aligned}$$

2.2.9 如图 2.13 所示电路, $A_0 = 5500$, 试求: (1) a、b 两端左侧的开路电压 U_{oc} 和等效电阻 R_0 ; (2) a、b 右侧接入电阻 $R_L = 2 \text{ k}\Omega$ 时, R_L 两端的电压 U_L 。

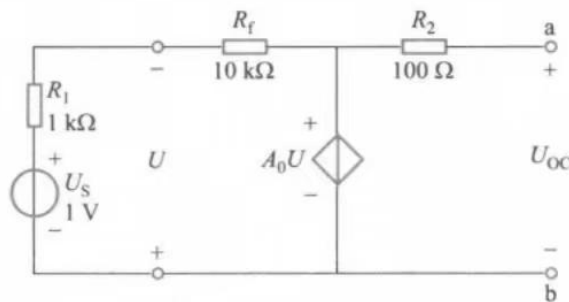



图 2.13 习题 2.2.9 电路

(1)

求开路电压:

$$\begin{cases} U_s - I(R_1 + R_f) - A_0 U = 0 \\ U = -(U_s - I R_1) \end{cases} \quad \begin{aligned} \therefore I &= \frac{U_s (A_0 + 1)}{R_1 (A_0 + 1) + R_f} \\ \therefore U_{oc} &= U_s - I(R_1 + R_2) = -9.98 \text{ V} \end{aligned}$$

求电阻：

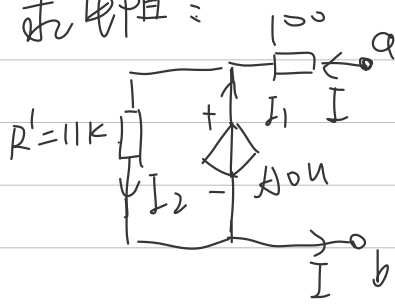

求 a,b 端短路电流

$$I_{短} = \frac{A_0 U}{R_2}$$

$$\therefore R_0 = \frac{U_{oc}}{I_{短}} = \frac{U_{oc} R_2}{A_0 U} = R_2 = 100 \Omega$$

$$(2) \quad U_L = \frac{U_{oc} R_L}{R_0 + R_L} = \frac{-9.98}{100 + 2K} \times 2K \Omega = -9.5 V$$