

3.1.3

$$(1) I_B = I_C / \beta = 1.5 / 80 \text{ mA} = 18.75 \mu\text{A}.$$

$$I_{EC} = I_B + I_C = (1.5 + 18.75 \times 10^{-3}) \text{ mA} = 1.51875 \text{ mA}.$$

$$U_{CB} = U_{CE} - U_{BE} = (6 - 0.7) \text{ V} = 5.3 \text{ V}.$$

$$\therefore R_B = U_{CB} / I_B = 283 \text{ k}\Omega.$$

$$R_C = (U_{CC} - U_{CE}) / I_{EC} = 12 / 1.51875 \text{ k}\Omega = 7.9 \text{ k}\Omega.$$

$$(2) \begin{cases} I_{EC} \cdot R_C + U_{CE} = U_{CC} \\ U_{CE} = I_B \cdot R_B + U_{BE} \end{cases}$$

$$I_B = I_C / \beta.$$

$$I_C + I_B = I_{EC}.$$

$$\Rightarrow I_C = 1.214 \text{ mA}$$

$$U_{CE} = 5.71 \text{ V}.$$

3.14.

(a) 是饱和失真, 可通过增大 R_B 或减小 R_C 消除.

(b) 是截止失真, 可通过减小 R_B 实现.

(c) 是两者都有, 需减小 U_i .


3.15

$$(1) I_B = \frac{U_{CC} - U_{BE}}{R_B} = \frac{12 - 0.7}{280 \times 10^3} \text{ A} = 40 \mu\text{A}.$$

$$I_C = \beta \cdot I_B = 50 \times 40 \times 10^{-6} \text{ A} = 2 \text{ mA}.$$

$$U_{CE} = U_{CC} - I_C \cdot R_C = 12 - 2 \times 3 = 6 \text{ V}.$$

(2)

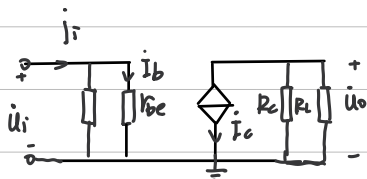

$$r_{be} = 200 + \frac{26}{I_E} (1 + \beta)$$

$$I_E = (1 + \beta) I_B$$

$$\therefore r_{be} = 850 \Omega.$$

$$u_o = I_C \cdot \frac{R_C \cdot R_L}{R_C + R_L}.$$

$$u_i = I_B \cdot r_{be}$$

$$A_u = -\frac{u_o}{u_i} = -88.2$$

$$r_i = \frac{u_i}{I_i} = u_i / [I_B (1 + \frac{R_C}{R_B})] = 0.84 \text{ k}\Omega.$$

$$r_o = R_C = 3 \text{ k}\Omega.$$

$$(3) I_C = \frac{U_{CC} - U_{CE}}{R_C} = 2.5 \text{ mA}$$


$$I_B = I_C / \beta = 50 \mu\text{A} \quad R_B = \frac{U_{CC} - U_{BE}}{I_B} = 226 \text{ k}\Omega.$$

$$(4) I_B = I_C / \beta = 30 \mu\text{A}$$

$$R_C = \frac{U_{CC} - U_{CE}}{I_C} = 4 \text{ k}\Omega \quad R_B = \frac{U_{CC} - U_{BE}}{I_B} = 370.7 \text{ k}\Omega$$

3.1.6

(1) 对电路进行戴维宁等效.

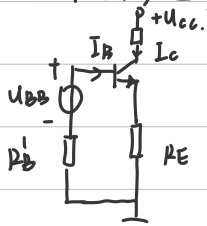

$$U_{BB} = U_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}} = 3V$$

$$R'_B = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 7.5 k\Omega$$

$$U_{EB} = U_{BE} + I_E R_E + I_B R'_B \quad I_E = (1+\beta) I_B$$


$$\therefore I_B = 0.019 mA \quad I_C = \beta I_B = 0.96 mA$$

$$U_{CE} = U_{CC} - I_C R_C - I_E R_E = 4.95 V$$

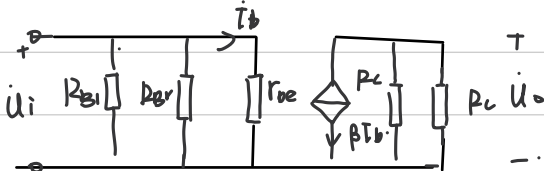(2) 画出微变等效模型:

$$r_{be} = 200 + \frac{26}{I_E} (1+\beta)$$

$$A_u = -\frac{U_o}{U_i} = -\frac{I_C R_C}{I_B r_{be}} = -64.5$$




$$(3) r_i = \left(\frac{1}{R_{B1}} + \frac{1}{R_{B2}} + \frac{1}{r_{be}} \right)^{-1} = 1.29 k\Omega$$

$$r_o = R_C = 5.1 k\Omega$$

3.1.7

(1) 对电路进行戴维宁等效.

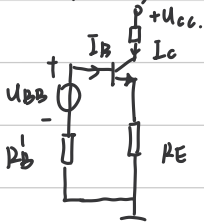

$$U_{BB} = U_{CC} \frac{R_{B2}}{R_{B1} + R_{B2}} = 3V$$


$$R'_B = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 7.5 k\Omega$$

$$U_{EB} = U_{BE} + I_E R_E + I_B R'_B \quad I_E = (1+\beta) I_B$$

$$\therefore I_B = 0.019 mA \quad I_C = \beta I_B = 0.96 mA$$

$$U_{CE} = U_{CC} - I_C R_C - I_E R_E = 4.95 V$$

(2) 画出微变等效电路.

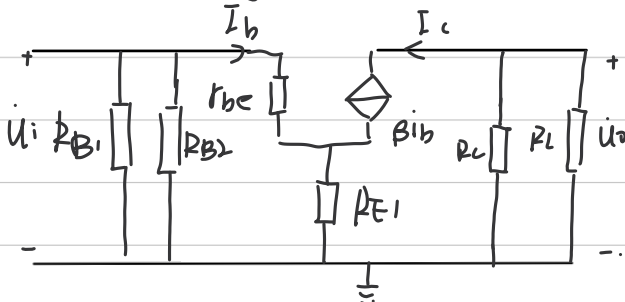


$$r_{be} = 200 + \frac{26}{I_E} (1+\beta)$$

$$A_u = -\frac{U_o}{U_i} = -\frac{I_C R_C}{I_B r_{be} + (1+\beta) I_B R_E} = -8.5$$

$$(3) r_i = \left(\frac{1}{R_{B1}} + \frac{1}{R_{B2}} + \frac{1}{r_{be} + (1+\beta) R_E} \right)^{-1} = 4.58 k\Omega$$

$$r_o = R_C = 5.1 k\Omega$$

3.1.8.

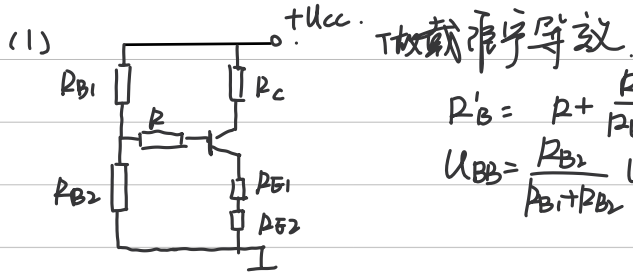


$$R'_B = R + \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 156 \text{ k}\Omega$$

$$U_{BB} = \frac{R_{B2}}{R_{B1} + R_{B2}} U_{CC} = 4.8 \text{ V}$$

$$I_B = \frac{U_{BB} - U_{BE}}{R'_B + (R_E + R_{E2})(1+\beta)} = 0.0159 \text{ mA}$$

$$I_C = \beta I_B = 0.795 \text{ mA} \quad I_E = (1+\beta) I_B = 0.81 \text{ mA}$$
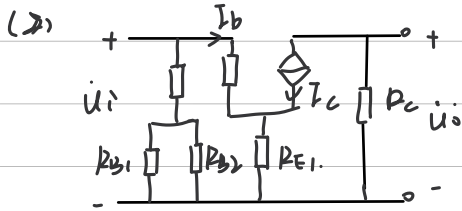
$$U_{CE} = U_{CC} - I_C R_C - I_E (R_{E1} + R_{E2}) = 6.33 \text{ V}$$



$$A_u = -\frac{u_o}{u_i} = \frac{-I_C R_C}{r_{be} + (1+\beta) R_{E1}} = -36.8$$

$$r_i = R + \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 6.64 \text{ k}\Omega \quad r_o = R_C = 5.1 \text{ k}\Omega$$

3.1.9.

等效电路

$$U_{BB} = \frac{R_{B2}}{R_{B1} + R_{B2}} U_{CC} = \frac{22}{43+22} \times 15 \text{ V} = 5.077 \text{ V}$$

$$R_B = \frac{R_{B1} R_{B2}}{R_{B1} + R_{B2}} = 14.55 \text{ k}\Omega$$

$$I_B = \frac{U_{BB} - U_{BE} - U_Z}{R_B} = 0.0946 \text{ mA} \quad I_C = \beta I_B = 5.676 \text{ mA}$$

$$U_{CE} = U_{CC} - I_C R_C - U_Z = 6.324 \text{ V}$$

(2)

$$A_u = -\frac{u_o}{u_i} = \frac{-I_C R_C}{I_B r_{be}} = -126.4$$

$$r_i = \left(\frac{1}{R_{B1}} + \frac{1}{R_{B2}} + \frac{1}{r_{be}} \right)^{-1} = 0.46 \text{ k}\Omega$$

$$r_o = R_C = 1 \text{ k}\Omega$$

